

Logic gates

→ Two types
of Logic gates

Basic logic gates (AND, OR, NOT)

universal logic gates (NAND, NOR)

→ Additional logic gates — EX-OR
EX-NOR

Def: Logic gates are fundamental building blocks of digital systems


NAND → NOT of AND

NOR → NOT of OR

The interconnection of gates to perform a variety of logical operations is called logic design

Basic gates

1) AND gate

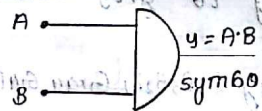

Truth Table


A	B	$Y = A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

Ex: 2 input AND gate

Other names → all or nothing gate

IC 7408 → four 2 input AND gate are available

OR gate

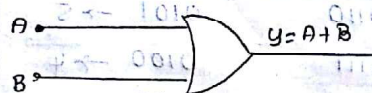


Truth Table

A	B	$Y = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

IC 7432 → four

2 input gates

Not gate (inverter)

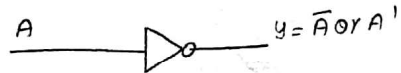


7404-size not gates


Truth Table

A	$y = \bar{A}$
0	1
1	0

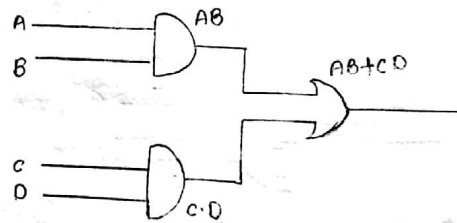
Draw the circuit for the given expression $F = AB + CD$



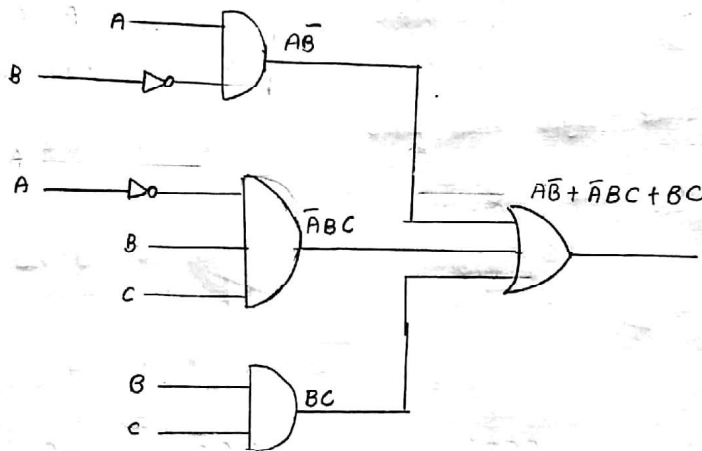Draw the circuit for given expression $\bar{F} = A\bar{B} + \bar{A}BC + BC$




$$F = (A+B) \cdot (C+\bar{D})$$

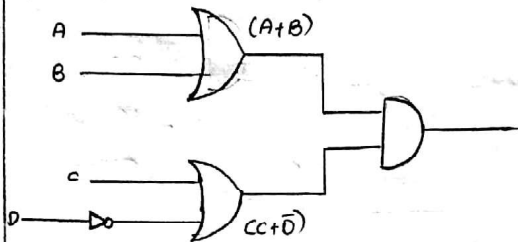


Universal logic gates:

NAND gate:

Truth table

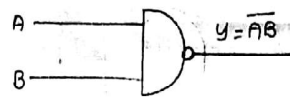

A	B	$\overline{AB}$
0	0	1
0	1	1
1	0	1
1	1	0

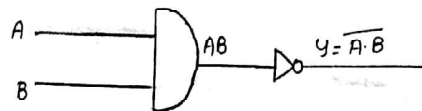


It is also called as bubbled OR gate

+ve ^{true} logic NAND gate is equivalent to -ve logic 'OR' gate


NOR gate

⇒ -ve true logic AND gate

⇒ Bubbled AND gate

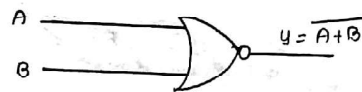


(or)

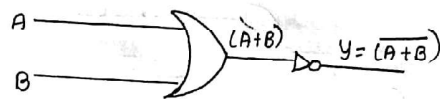

Truth Table

A	B	$y = \overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

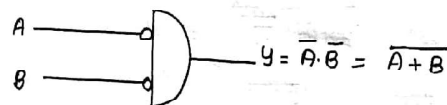


Demorgan's law:

$$\overline{A+B} = \overline{A} \cdot \overline{B}$$

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

Ex-OR gate:

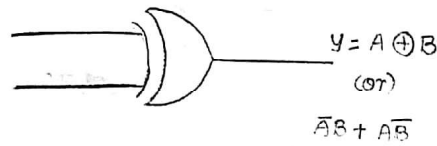


Truth Table

A	B	$Y = A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

$Y = '1'$ when there is odd no. of 1's in input otherwise '0'

Ex-NOR gate

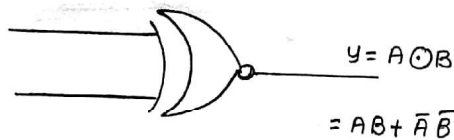

Truth Table

A	B	$Y = A \odot B$
0	0	1
0	1	0
1	0	0
1	1	1

Bubbled OR gate $\rightarrow$ NAND Gate

Bubbled NAND gate $\rightarrow$ Bubbled OR gate

Bubbled AND gate $\rightarrow$ NOR gate


Bubbled NOR gate $\rightarrow$ AND gate

Realisation of logic gates

1. using NAND gate:


AND gate

$$Y = A \cdot B$$

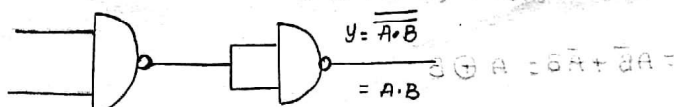

2) NOT gate:

$$Y = \bar{A}$$

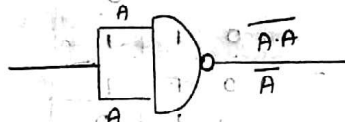


3) OR gate:

$$Y = A + B$$


$$= \overline{\overline{A+B}}$$

$$= \overline{\bar{A} \cdot \bar{B}}$$

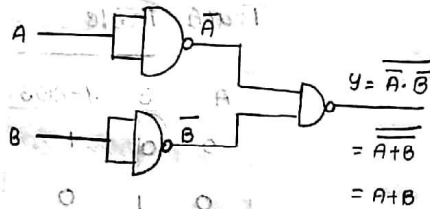

4. EX-OR gate

$$Y = \bar{A}B + A\bar{B}$$

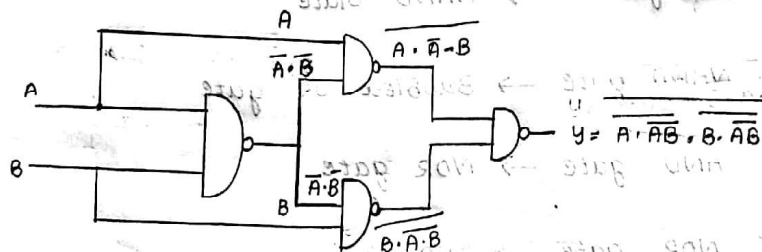

$$Y = \overline{A \cdot \bar{A} \cdot \bar{B}} \cdot \bar{B} \cdot \bar{A} \cdot \bar{B}$$

$$= (\overline{A \cdot \bar{A} \cdot \bar{B}}) + (\overline{B \cdot \bar{A} \cdot \bar{B}})$$


$$= (A \cdot \bar{A} \cdot \bar{B}) + (B \cdot \bar{A} \cdot \bar{B})$$

$$= [(A \cdot (\bar{A} + \bar{B})) + (B \cdot (\bar{A} + \bar{B}))]$$

$$= (A \cdot \bar{A}) + (A \cdot \bar{B}) + (\bar{A} \cdot B) + (B \cdot \bar{B})$$

$$= A\bar{B} + \bar{A}B = A \oplus B$$

Ex-NOR gate

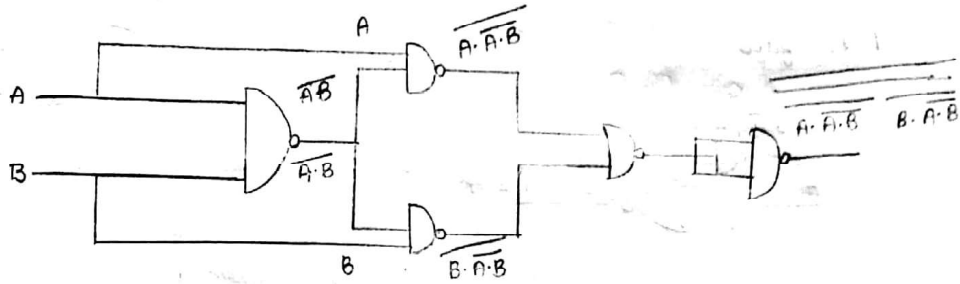

$$Y = A \cdot \overline{A} \cdot B \cdot \overline{B} \cdot A \cdot B$$

$$= \overline{A \cdot A \cdot B} \cdot \overline{B \cdot A \cdot B}$$

$$= \overline{A \cdot (\bar{A} + \bar{B})} \cdot \overline{B \cdot (\bar{A} + \bar{B})}$$

$$= \overline{A} + (\overline{A+B}) \cdot \overline{B} + (\overline{A+B})$$

$$= [\bar{A} + \overline{\bar{A} \cdot \bar{B}}] \cdot [\bar{B} + (\bar{A} \cdot \bar{B})]$$

$$= [\bar{A} + AB] [\bar{B} + (AB)]$$


$$= \overline{A}\overline{B} + \underbrace{\overline{A}AB}_{0} + \underbrace{AB\overline{B}}_{0} + ABAB$$

$$Y = \bar{A}\bar{B} + AB$$

$$Y = A \odot B$$

$$\left. \begin{array}{l} A \cdot \bar{A} = 0 \\ A \cdot A = A \end{array} \right\} \text{boolean laws}$$


NOR gate

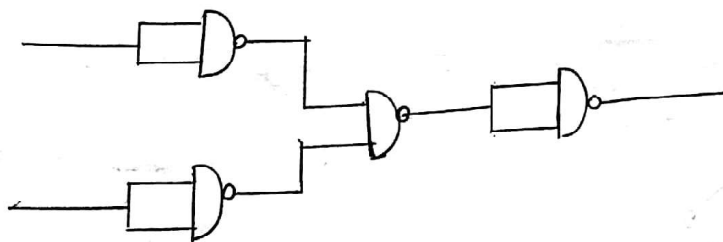

NOR gate


1. NOT gate

$$Y = \bar{A}$$

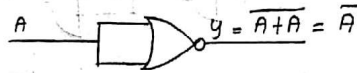

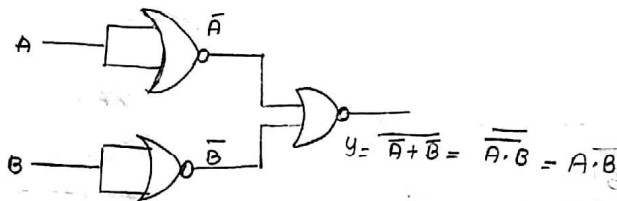
2. AND gate

$$Y = A \cdot B = \overline{\overline{A \cdot B}} = \overline{\overline{A} + \overline{B}}$$



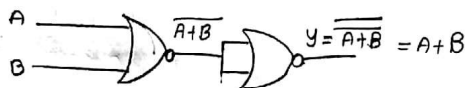
3. OR gate

$$Y = A + B = \overline{\overline{A + B}}$$




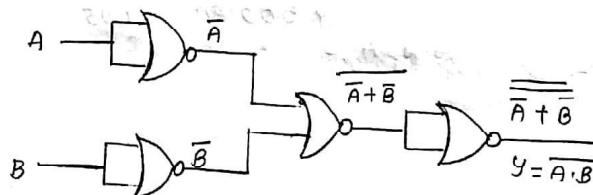4. NAND gate

$$Y = \overline{A \cdot B} = \overline{\overline{\overline{A \cdot B}}} = \overline{\overline{A} + \overline{B}}$$



5. EX-OR gate


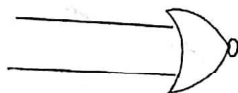



NAND- NAND and NOR- NOR implementation

I) using NAND



1. Draw the circuit using basic gates
2. If NAND hardware has been chosen add bubbles at the output of each AND gate and add bubbles at the inputs of OR gate
3. If NOR hardware has been chosen add bubbles at the output of OR gate and add bubbles at the inputs of each AND gate.
4. Add an inverter (NOT gate) on each line receive a bubble in step 2 and 3.
5. Replace bubbled OR gate by NAND gate and bubbled AND gate by NOR gate.
6. Eliminate double inversions.

Eg:- $f = AB + C$



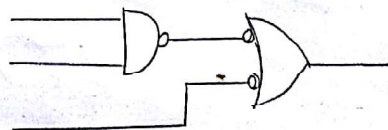
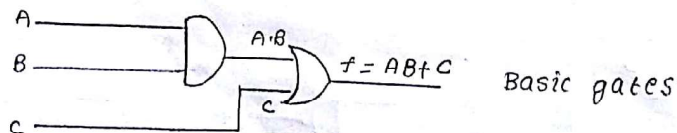


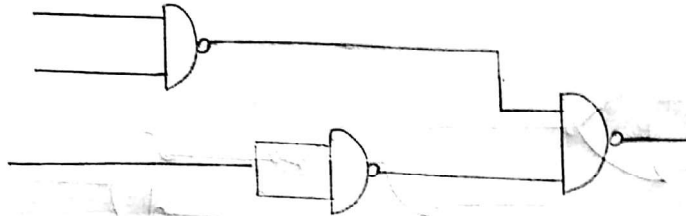

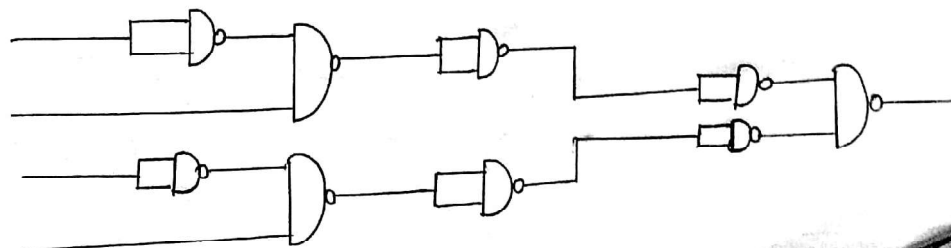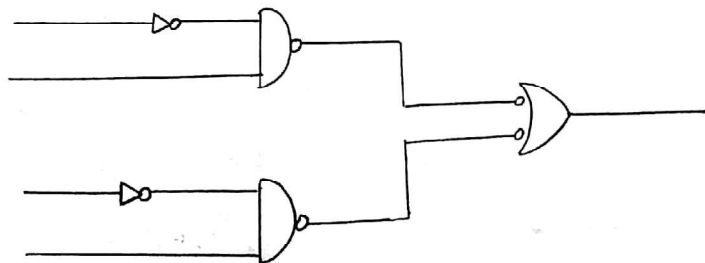$f = \bar{A}B + \bar{B}C$ using only NAND gates



2)

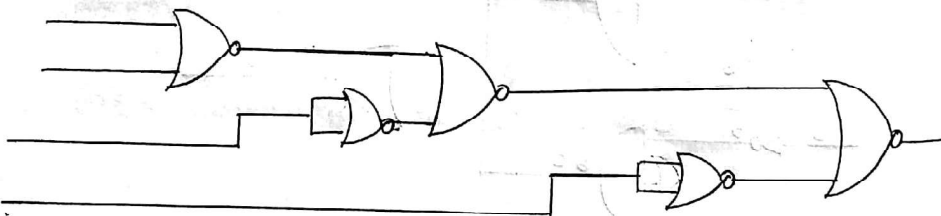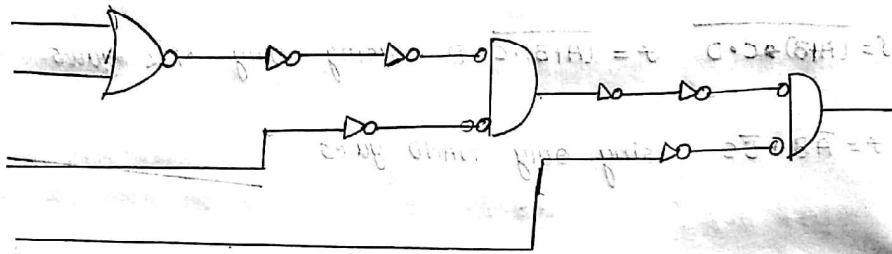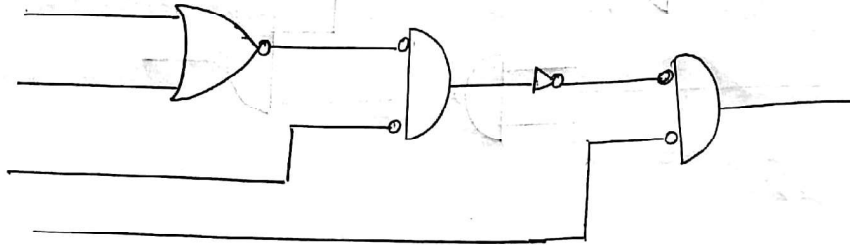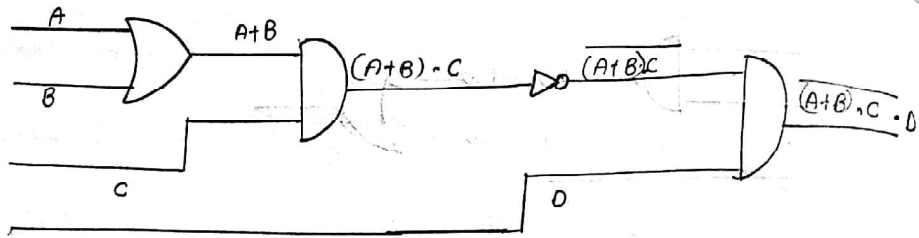

Boolean algebra and

Minimization techniques

Concepts

- Boolean theorems
- Simplification or minimization using Boolean algebra
- Standard SOP & POS
- Karnaugh maps
- 2, 3, 4, 5, 6 - variable k-maps.

Boolean algebra is a system of mathematical logic. It is an algebraic system consisting of a set of elements $\{0, 1\}$ with two binary operators 'OR' & 'AND' and a unary operator 'NOT'.

It is a basic mathematical tool in the analysis and synthesis of switching circuits.

It is a way to express logic functions algebraically.

Any complex logic statements can be expressed by a Boolean function.

Boolean algebra

Boolean laws and theorems

1. AND laws

$$A \cdot 0 = 0$$

$$A \cdot 1 = A$$

$$A \cdot \bar{A} = 0$$

$$A \cdot A = A$$

2. OR laws

$$A + 0 = A$$

$$A + 1 = 1$$

$$A + \bar{A} = 1$$

$$A + A = A$$

3. Absorption laws

$$A + AB = A$$

$$A(A+B) = A$$

4. Reducant laws

$$A + \bar{A}B = A + B$$

$$A(\bar{A} + B) = AB$$

5. Commutative law

$$A + B = B + A$$

$$AB = BA$$

6. Distributive law

$$A(B+C) = AB + AC$$

$$A + (BC) = (A+B)(A+C)$$

7. Associative law

$$(A+B)+C = A+(B+C)$$

$$(AB)C = A(BC)$$

8. Demorgan's law:

$$\overline{A+B} = \bar{A} \cdot \bar{B}$$

$$\overline{A \cdot B} = \bar{A} + \bar{B}$$

Ex:- Prove $A(B+C) = AB + AC$

A	B	C	B+C	A(B+C)	AB	AC	AB+AC
0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	1	1	1	0	1	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

Simplify the following expansion

1. $x(x+y+z)$

By absorption law

$$x(x+y+z) = x$$

2. $AB+BC+C$

$$= AB+C(B+1)$$

$$= AB+C(1)$$

$$= AB+C$$

3. $ABC + AB\bar{C} + A\bar{B}C$

$$= A(BC + B\bar{C} + \bar{B}C)$$

$$= A[B(C+\bar{C}) + \bar{B}C]$$

$$= A(B + \bar{B}C)$$

$$= A(B + C)$$

4. $\overline{ABC} + \overline{AB}C + A\bar{B}\bar{C}$

$$= \overline{AB} + \bar{C} + \overline{AB}C + A\bar{B}\bar{C}$$

$$= \overline{AB} (1+C) + \bar{C} + A\bar{B}\bar{C}$$

$$= \overline{AB} (1) + \bar{C} + A\bar{B}\bar{C}$$

$$= \overline{AB} + \bar{C} + A(\bar{B} + \bar{C})$$

$$= \overline{AB} + A\bar{B} + A\bar{C}$$

$$= \overline{AB} + A\bar{B} + \bar{C}$$

$$= \bar{A} + \bar{B} + A\bar{B} + \bar{C}$$

$$= \bar{A} + \bar{B} + \bar{C}$$

$$4. A+B+C+D+E+1$$

$$= 1$$

$$5. Y = A \cdot \bar{A}C$$

$$= 0$$

$$6. x\bar{y}\bar{z} + \bar{y}\bar{z} + x$$

$$= \bar{y}\bar{z}(x+1) + x$$

$$= \bar{y}\bar{z} + x$$

$$7. A(A+B)$$

$$= AA + AB$$

$$= A + AB$$

$$= A(1)$$

$$= A$$

$$8. AB + \bar{A}B + BC$$

$$= B(A + \bar{A}) + BC$$

$$= B + BC = B(1+C) = B$$

Boolean theorems

$$1. AB + \bar{A}C + BC = AB + \bar{A}C \text{ [consensus theorem]}$$

$$AB + \bar{A}C + BC = AB + \bar{A}C + [BC \cdot 1]$$

$$= AB + \bar{A}C + BC[A + \bar{A}]$$

$$= AB + \bar{A}C + ABC + \bar{A}BC$$

$$= AB(1+C) + \bar{A}C(1+B)$$

$$= AB + \bar{A}C$$

$$2. (A+B) \cdot (\bar{A}+C) \cdot (B+C) = (A+B)(\bar{A}+C)$$

$$(A+B)(\bar{A}+C)(B+C) = (A\bar{A} + AC + AB + BC)(B+C)$$

$$= ABC + AC + \bar{A}B + \bar{A}BC + BC + BC$$

$$= BC(A + \bar{A} + 1 + 1) + AC + \bar{A}B$$

$$= BC + AC + \bar{A}B$$

$$(A+B)(\bar{A}+C) = A\bar{A} + AC + \bar{A}B + BC$$

$$= AC + \bar{A}B + BC$$

$$\therefore LHS = RHS$$

Transposition theorem

$$1. AB + \bar{A}C = (A+C)(\bar{A}+B)$$

$$= A\bar{A} + AB + \bar{A}C + BC$$

$$= AB + \bar{A}C + BC$$

$$= AB + \bar{A}C + [BC \cdot 1]$$

$$= AB + \bar{A}C + BC[A + \bar{A}] = AB + \bar{A}C + ABC + \bar{A}BC$$

$$= AB[1+C] + \bar{A}C[1+B]$$

$$= AB + \bar{A}C$$

Minimise the given Boolean expansion

$$1. f = AB + \bar{A}B + \bar{A}\bar{B}$$

$$= AB + \bar{A}(B + \bar{B})$$

$$= AB + \bar{A}$$

$$= \bar{A} + B$$

$$2. f = A[B + \bar{C}(\overline{AB + A\bar{C}})]$$

$$= A[B + \bar{C}(\bar{A}\bar{B} + \bar{A}\bar{C})]$$

$$= A[B + \bar{C}[(\bar{A} + \bar{B})(\bar{A} + \bar{C})]]$$

$$= A[B + \bar{C}[\bar{A}C + \bar{B}\bar{A} + \bar{B}\bar{C}]]$$

$$= A[B + \bar{A}\bar{B}\bar{C}] = AB$$

$$3. f = \bar{A}\bar{B}C + A\bar{B}C + \bar{A}BC + ABC + \bar{A}\bar{B}\bar{C}$$

$$= \bar{B}C(\bar{A} + A) + BC(\bar{A} + A) + \bar{A}\bar{B}\bar{C}$$

$$= \bar{B}C + BC + \bar{A}\bar{B}\bar{C}$$

$$= \bar{B}(C + \bar{A}\bar{C}) + BC = \bar{B}(C + \bar{A}) + BC$$

$$= \bar{B}C + \bar{A}\bar{B} + BC = \bar{A}\bar{B} + C$$

$$4. f = (x+y)(\bar{x}z+z)(\bar{y}+xz)$$

$$= (xz + y\bar{x}z + yz)(\bar{y} + xz)$$

$$= x\bar{y}z + xz + xyz$$

$$= x\bar{y}z + xz(1+y)$$

$$= xz(1+y)$$

$$= xz$$

ABC	Max terms (M_i)	min terms (m_i)
0 0 0	$A+B+C \rightarrow m_0$	$\bar{A} \cdot \bar{B} \cdot \bar{C} \rightarrow m_0$
0 0 1	$A+B+\bar{C} \rightarrow m_1$	$\bar{A} \cdot \bar{B} \cdot C \rightarrow m_1$
0 1 0	$A+\bar{B}+C \rightarrow m_2$	$\bar{A} \cdot B \cdot \bar{C} \rightarrow m_2$
0 1 1	$A+\bar{B}+\bar{C} \rightarrow m_3$	$\bar{A} \cdot B \cdot C \rightarrow m_3$
1 0 0	$\bar{A}+B+C \rightarrow m_4$	$A \cdot \bar{B} \cdot \bar{C} \rightarrow m_4$
1 0 1	$\bar{A}+B+\bar{C} \rightarrow m_5$	$A \cdot \bar{B} \cdot C \rightarrow m_5$
1 1 0	$\bar{A}+\bar{B}+C \rightarrow m_6$	$A B \bar{C} \rightarrow m_6$
1 1 1	$A+B+C \rightarrow m_7$	$A B C \rightarrow m_7$

Note: A

$\bar{A}$

0

1

1

0

Eg.: $f = \bar{A}B + A\bar{B}$ (sum of products) can also be expressed as $(\bar{A}+B)(A+\bar{B})$

	A	B	$f = \bar{A}B + A\bar{B}$
$\bar{A}\bar{B}$	0	0	1
$\bar{A}B$	0	1	1
$A\bar{B}$	1	0	0
AB	1	1	0

$$f(A,B) = \bar{A}\bar{B} + \bar{A}B$$

$$= m_0 + m_1$$

$$= \sum m(0,1)$$

$$f(A,B) = (\bar{A}+B) \cdot (\bar{A}+\bar{B})$$

$$= M_2 \cdot M_3$$

$$= \Pi M(2,3)$$

→ Converting normal SOP into standard SOP

1. Find out missing literal

2. AND (.) the missing literal with its complement

3. Expand the terms and reorder the literals

4. Neglect the repeated terms

Eg:- $f = AB + \bar{B}C$

$$f = AB \cdot (C + \bar{C}) + \bar{B}C \cdot (A + \bar{A})$$

$$= ABC + AB\bar{C} + A\bar{B}C + \bar{A}\bar{B}C$$

$$= 111 + 110 + 101 + 001$$

$$= m_7 + m_6 + m_5 + m_1$$

$$= \sum m(7,6,5,1) = \sum m(1,5,6,7)$$

ii) $f(A,B) = \bar{A} + \bar{B}$

$$= \bar{A} \cdot (B + \bar{B}) + \bar{B} \cdot (A + \bar{A})$$

$$= \bar{A}B + \bar{A}\bar{B} + A\bar{B} + \bar{A}\bar{B}$$

$$= \bar{A}B + A\bar{B} + \bar{A}\bar{B}$$

$$= 01 + 10 + 00$$

$$= m_1 + m_2 + m_0$$

$$= \sum m(0,1,2)$$

iii) $f(A,B,C) = \bar{A}B + \bar{A}BC + A\bar{B} + A\bar{B}C$

$$= \bar{A}B \cdot (C + \bar{C}) + \bar{A}\bar{B}C + A\bar{B} \cdot (C + \bar{C}) + A\bar{B}C$$

$$= \bar{A}BC + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}C + A\bar{B}\bar{C} + A\bar{B}C$$

$$= \bar{A}BC + \bar{A}B\bar{C} + A\bar{B}C + A\bar{B}\bar{C}$$

$$= 011 + 010 + 101 + 100$$

$$= m_3 + m_2 + m_5 + m_4$$

$$= \sum m(2, 3, 4, 5)$$

$$f(A, B, C, D) = AB + BCD + \bar{B}\bar{C}\bar{D}$$

$$= AB \cdot (\bar{C} + C) \cdot (\bar{D} + D) + BCD(\bar{A} + A) + \bar{B}\bar{C}\bar{D}(\bar{A} + A)$$

$$= AB \cdot [\bar{C}\bar{D} + \bar{C}D + C\bar{D} + CD] + BCD\bar{A} + ABCD + A\bar{B}CD + A\bar{B}\bar{C}\bar{D}$$

$$= AB\bar{C}\bar{D} + AB\bar{C}D + AB\bar{C}D + ABC\bar{D} + \bar{A}BCD + ABCD + A\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}\bar{D}$$

$$= AB\bar{C}\bar{D} + AB\bar{C}D + AB\bar{C}D + \bar{A}BCD + ABCD + A\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}\bar{D}$$

$$= 1100 + 1101 + 1110 + 0111 + 1111 + 1000 + 0000$$

$$= m_{12} + m_{13} + m_{14} + m_7 + m_{15} + m_8 + m_0$$

$$= \sum m(0, 7, 8, 12, 13, 14, 15)$$

$$f(A, B, C) = \bar{A} + BC$$

$$= \bar{A} \cdot (B + \bar{B}) \cdot (C + \bar{C}) + BC(A + \bar{A})$$

$$= \bar{A} \cdot (BC + B\bar{C} + \bar{B}C + \bar{B}\bar{C}) + BCA + BC\bar{A}$$

$$= \bar{A}BC + \bar{A}B\bar{C} + \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + ABC + \bar{A}BC$$

$$= \bar{A}BC + \bar{A}B\bar{C} + \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + \bar{A}BC + \bar{A}BC$$

$$= 011 + 010 + 001 + 000 + 111 + 111$$

$$= m_3 + m_2 + m_1 + m_0 + m_7$$

$$= \sum m(0, 1, 2, 3, 7)$$

Converting normal POS into standard POS

1. Find out the missing literal

→ OR (+) the sum term with the missing literal (.) its complement

→ Expand the terms using distributive law and reorder the literals

→ neglect the repeated terms

$$f = (A+B)(\bar{B}+C)$$

$$= [(A+B) + (C \cdot \bar{C})] \cdot [(\bar{B}+C) + (A \cdot \bar{A})]$$

$$= (A+B+C)(A+B+\bar{C}) \cdot (\bar{B}+C+A)(\bar{B}+C+\bar{A})$$

$$= (000, 001, 010, 011, 100, 101, 110, 111)$$

$$= \sum \pi M(0, 1, 2, 6)$$

$$f(A, B, C) = (A+\bar{B}+C)(A+\bar{B})(\bar{B}+C)$$

$$= (A+\bar{B}+C) [(A+\bar{B}) + (C \cdot \bar{C})] \cdot [(\bar{B}+C) + (A \cdot \bar{A})]$$

$$= (A+\bar{B}+C) [A+\bar{B}+C] \cdot (A+\bar{B})(\bar{B}+C)$$

$$= (A+\bar{B}+C)(A+\bar{B}+C)(\bar{B}+C)$$

$$= (010, 011, 111)$$

$$= \sum \pi M(2, 3, 7)$$

$$f(A, B, C, D) = (A+B+C+D)(A+\bar{B}+C)$$

$$= (A+B+C+D) [(A+\bar{B}+C) + (D \cdot \bar{D})]$$

$$= (A+B+C+D) [A+\bar{B}+C+D]$$

$$= (0001, 0100, 0101)$$

$$= \sum \pi M(1, 4, 5)$$

Expand the function output $f = A\bar{B}C + \bar{A}\bar{B} + \bar{B}\bar{C}$ to min terms

and max terms

$$f = A\bar{B}C + \bar{A}\bar{B} + \bar{B}\bar{C}$$

$$= A\bar{B}C + \bar{A}\bar{B} \cdot (C + \bar{C}) + \bar{B}\bar{C}(A + \bar{A})$$

$$= A\bar{B}C + \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C}$$

$$= A\bar{B}C + \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C}$$

$$= (101) + (001) + (000) + (100)$$

$$= \sum m(0, 1, 4, 5)$$

$$= \pi M(2, 3, 6, 7)$$

$$f(A, B) = (\bar{A})(\bar{B})$$

$$= [(\bar{A}) + (B \cdot B)] [(\bar{B}) + (A \cdot \bar{A})]$$

$$= (\bar{A} + B)(\bar{A} + \bar{B})(\bar{B} + A)(\bar{B} + \bar{A})$$

$$= (\bar{A} + B)(\bar{A} + \bar{B})(\bar{B} + A)$$

$$= (010) + (011) + (001) + (000)$$

$$= \pi M(1, 2, 3)$$

$$f(A, B, C, D) = (A + B + C + \bar{D})(A + B + C)$$

$$= (A + B + C + \bar{D})[(A + B + C) + (D \cdot \bar{D})]$$

$$= (A + B + C + \bar{D})(A + B + C + D)(A + B + C + \bar{D})$$

$$= (A + B + C + \bar{D})(A + B + C + D)(\bar{D} + D + \bar{D} + D)$$

$$= (0000)(0001)$$

$$= \pi M(0, 1)$$

Duality and complements of Boolean expression

duality

$$AND(\cdot) \rightarrow OR(+)$$

$$OR(+)\rightarrow AND(\cdot)$$

$$0 \rightarrow 1$$

$$1 \rightarrow 0$$

complement

$$AND(\cdot) \rightarrow OR(+)$$

$$OR(+)\rightarrow AND(\cdot)$$

$$0 \rightarrow 1$$

$$1 \rightarrow 0$$

$$A \rightarrow \bar{A}$$

$$\bar{A} \rightarrow A$$

Find the duality and complement of given function

$$F = (\bar{A}B) + (\bar{B}C) + (ABC)$$

Duality

$$F = (\bar{A}+B) \cdot (\bar{B}+C) + (A+B+C)$$

Complement

$$f = (A+\bar{B}) \cdot (B+\bar{C}) \cdot (\bar{A}+\bar{B}+\bar{C})$$

Eg:-

$$\text{duality } 0 \cdot 1 = 0$$

$$0 + 1 = 1$$

Karnaugh map (k-map):

2, 3, 4, 5, 6 variable k-map

A	B	$\bar{B}$	B
	$\bar{A}$	0	1
A	$\bar{A}$	2	3

2 variable k-map

A	BC	$\bar{B}\bar{C}$	$\bar{B}C$	BC	$B\bar{C}$
	$\bar{A}$	0	1	3	2
A	$\bar{A}$	4	5	7	6

3-variable k-map

AB \ CD	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	0	1	3	2
$\bar{A}B$	4	5	7	6
$A\bar{B}$	12	13	15	14
AB	8	9	11	10

Eq: $f(A, B) = \bar{A}B + \bar{A}\bar{B} + A\bar{B}$

$$= \bar{A}(B + \bar{B}) + A\bar{B}$$

$$= \bar{A} + A\bar{B}$$

$$= \bar{A} + \bar{B}$$

A \ B	$\bar{B}$	B
$\bar{A}$	1	0
A	0	0

$$f = \bar{B}(\bar{A} + A) + \bar{A}\bar{B}(\bar{B} + B)$$

$$= \bar{B} + \bar{A}(\bar{B} + B)$$

$$= \bar{A} + \bar{B}$$

$$f = \bar{A}B + AB + A\bar{B}$$

$$= B(A + \bar{A}) + A\bar{B}$$

$$= B + A$$

A \ B	$\bar{B}$	B
$\bar{A}$	0	1
A	1	1

$$f = B(\bar{A} + A) + A(\bar{B} + B)$$

$$= A + B$$

$f = \sum m(0, 1, 6, 7)$ Reduce using k-map

BC \ A	$\bar{B}\bar{C}$	$\bar{B}C$	$B\bar{C}$	BC
$\bar{A}$	0	1	0	0
A	0	0	1	1

$$f = \bar{A}(\bar{B}\bar{C} + \bar{B}C) + A(B\bar{C} + BC)$$

$$= \bar{A}(\bar{B}(\bar{C} + C)) + A(B(\bar{C} + C))$$

$$= \bar{A}\bar{B} + AB$$

$$f(A, B, C) = \sum m(0, 1, 4, 5)$$

A \ BC	$\overline{B}\overline{C}$	$\overline{B}C$	$B\overline{C}$	BC
$\overline{A}$	0	1	3	2
A	4	5	7	6

$$\begin{aligned} f &= (\overline{A} + A) \cdot (\overline{B}\overline{C} + \overline{B}C) \\ &= 1 \cdot \overline{B}(\overline{C} + C) \\ &= \overline{B} \end{aligned}$$

$$f(A, B, C) = \sum m(0, 1, 5, 7)$$

A \ BC	$\overline{B}\overline{C}$	$\overline{B}C$	$B\overline{C}$	BC
$\overline{A}$	0	1	3	2
A	4	5	7	6

$$\begin{aligned} f &= \overline{A}(\overline{B}\overline{C} + \overline{B}C) + A(\overline{B}C + BC) \\ &= \overline{A}(\overline{B}(\overline{C} + C)) + A(C(\overline{B} + B)) \\ &= \overline{A}\overline{B} + AC \end{aligned}$$

$$f(A, B, C, D) = \sum m(1, 3, 5, 7, 12, 14)$$

AB \ CD	$\overline{C}\overline{D}$	$\overline{C}D$	$C\overline{D}$	CD
$\overline{A}\overline{B}$	0	1	3	2
$\overline{A}B$	4	5	7	6
$A\overline{B}$	12	13	15	14
AB	8	9	11	10

$$\begin{aligned} f &= (\overline{A}\overline{B} + \overline{A}B) \cdot (\overline{C}\overline{D} + C\overline{D}) + AB(\overline{C}\overline{D} + CD) \\ &= [\overline{A}(\overline{B} + B)] \cdot [\overline{D}(\overline{C} + C)] + AB[\overline{C}\overline{D} + CD] \\ &= \overline{A} \cdot \overline{D} + AB\overline{D} \\ &= \overline{A}\overline{D} + AB\overline{D} \end{aligned}$$

$$f(A, B, C, D) = \sum m(0, 2, 3, 8, 10, 11, 12, 14)$$

AB \ CD	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	0	1	1	1
$\bar{A}B$	0	0	0	0
$A\bar{B}$	1	0	0	1
AB	1	0	1	1

$$(\bar{A}\bar{B} + A\bar{B}) \cdot (CD + C\bar{D}) + (\bar{A}B + AB) \cdot (\bar{C}\bar{D} + C\bar{D}) + (\bar{A}\bar{B} + A\bar{B}) (\bar{C}\bar{D} + C\bar{D})$$

$$[\bar{B}(A + \bar{A})] \cdot [C(\bar{D} + D)] + [A(B + \bar{B})] \cdot [\bar{D}(\bar{C} + C)] + [\bar{B}(A + \bar{A})] (\bar{D}(\bar{C} + C))$$

$$\bar{B}C + A\bar{D} + \bar{B}\bar{D}$$

$$f(A, B, C, D) = \sum m(0, 1, 2, 3, 9, 11, 12, 13, 14)$$

K-map using don't care combinations

$$f(A, B, C) = \sum m(1, 3, 5) + \sum \alpha(7)$$

A \ BC	$\bar{B}\bar{C}$	$\bar{B}C$	$B\bar{C}$	BC
$\bar{A}$	0	1	1	0
A	0	1	X	1

↓

A \ BC	$\bar{B}\bar{C}$	$\bar{B}C$	$B\bar{C}$	BC
$\bar{A}$	0	1	1	0
A	0	1	1	0

X - '1' - pair, quad, or an octane
X - '0'

$$\text{Quad} = (\bar{A} + A) \cdot (\bar{B}C + B\bar{C}) = C$$

$$f(A, B, C, D) = \sum m(1, 3, 7, 11, 15) + \sum d(0, 2, 4)$$

$\backslash CD$	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	0	1	3	2
$\bar{A}B$	4	5	7	6
$A\bar{B}$	12	13	15	14
AB	8	9	11	10

$\backslash CD$	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	1	1	1	1
$\bar{A}B$	0	0	1	0
$A\bar{B}$	0	0	1	0
AB	0	0	1	0

$$(\bar{A}\bar{B} + \bar{A}B + A\bar{B} + AB) \cdot CD + \bar{A}\bar{B}(\bar{C}\bar{D} + \bar{C}D + CD + C\bar{D})$$

$$= (\bar{A} + A) \cdot CD + \bar{A}\bar{B}(\bar{C} + C)$$

$$= CD + \bar{A}\bar{B}$$

$$f(A, B, C, D) = \sum m(0, 7, 8, 9, 10, 12) + \sum d(2, 5, 13)$$

$\backslash CD$	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	0	1	3	2
$\bar{A}B$	4	5	7	6
$A\bar{B}$	12	13	15	14
AB	8	9	11	10

$\backslash CD$	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	1	0	0	1
$\bar{A}B$	0	1	1	0
$A\bar{B}$	1	1	0	0
AB	1	1	0	1

$$= (\bar{A}\bar{B} + \bar{A}B) \cdot (\bar{C}\bar{D} + \bar{C}D) + (\bar{A}\bar{B} + A\bar{B}) \cdot (\bar{C}D + C\bar{D}) + \bar{A}B(\bar{C}D + CD)$$

$$= \bar{A}\bar{C} + \bar{B}\bar{D} + \bar{A}BD$$

$$f(A, B, C, D) = \prod M(0, 3, 4, 7, 8, 10, 12, 14) + \prod d(2, 6)$$

$\backslash CD$	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	0	1	3	2
$\bar{A}B$	4	5	7	6
$A\bar{B}$	12	13	15	14
AB	8	9	11	10



$\backslash CD$	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	0	1	0	0
$\bar{A}B$	0	1	0	0
$A\bar{B}$	0	1	1	0
AB	0	1	1	0